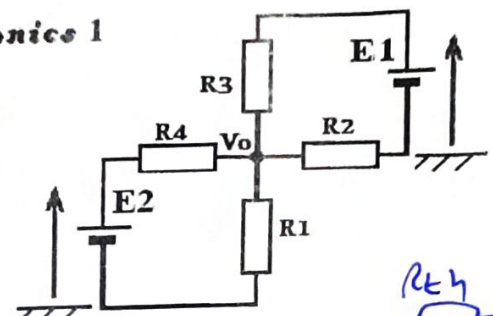




الاسم: _____
 اللقب: _____
 الشعبة: _____
 الفوج: _____

Exam (1h:30min)
Fundamental Electronics 1

5pts. Exercise 1: Lets consider the opposite circuit:
 Select one method to **determinate** the output voltage?
 Choose from: (Superposition, Thevenin, or Milman)




MILMAN

$$V_o = \frac{E_2 \cdot \frac{1}{R_4} + E_1 \cdot \frac{1}{R_3}}{\frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2}} \quad (2)$$

$$V_o = \frac{R_1 R_2 (R_3 E_2 + R_4 E_1)}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_3 R_4} \quad (3)$$

Superposition

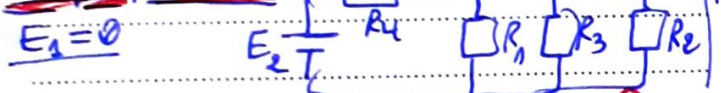

Voltage divider $\Rightarrow V_o^{(1)} = \frac{R_1 R_2 R_3}{R_1 R_2 R_3 + R_4} E_2$ (1)

$$\Rightarrow V_o^{(1)} = \frac{R_1 R_2 R_3 E_2}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_3 R_4} \quad (1)$$



Voltage divider $V_o^{(2)} = \frac{R_1 R_2 R_4}{R_1 R_2 R_4 + R_3} E_1$ (1)

$$\Rightarrow V_o^{(2)} = \frac{R_1 R_2 R_4 E_1}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_3 R_4} \quad (1)$$

So $V_o = V_o^{(1)} + V_o^{(2)} = \frac{R_1 R_2 (R_3 E_2 + R_4 E_1)}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_3 R_4}$ (1)

Thevenin

$V_{o(D)} \Rightarrow V_o = \frac{R_1 E_{th}}{R_2 + R_{th}}$ (a) (1)

$R_{th} = R_2 \parallel R_3 \parallel R_4 = \frac{R_2 R_3 R_4}{R_2 R_3 + R_2 R_4 + R_3 R_4}$ (1) (b)

MILMAN

$\Rightarrow E_{th} = \frac{E_2}{\frac{1}{R_4} + \frac{1}{R_3}}$ (1) (c)

$\Rightarrow E_{th} = \frac{R_2 (R_3 E_2 + R_4 E_1)}{R_2 R_3 + R_3 R_4 + R_2 R_4}$ (1) (c)

(b) and (c) with (a) \Rightarrow

$$V_o = \frac{R_1 R_2 (R_3 E_2 + R_4 E_1)}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_3 R_4} \quad (1)$$

5pts. Exercise 2:


Lets consider the opposite quadrupole circuit:

1/ **Determinate** the admittance matrix **[Y]** using **parallel** association?

$[Y] = [Y1] + [Y2] = \begin{pmatrix} \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R} & -\frac{1}{2R} \\ -\frac{1}{2R} & \frac{3}{2R} \end{pmatrix} + \begin{pmatrix} \frac{2R}{3R^2} = \frac{2}{3R} & -\frac{R}{3R^2} = -\frac{1}{3R} \\ -\frac{1}{3R} & \frac{2}{3R} \end{pmatrix} = \begin{pmatrix} \frac{3}{2R} + \frac{2}{3R} = \frac{13}{6R} & -\frac{1}{2R} - \frac{1}{3R} = -\frac{5}{6R} \\ -\frac{5}{6R} & \frac{13}{6R} \end{pmatrix}$ (1) (1)


2/ **Determinate** its hybrid matrix? **[H]**=

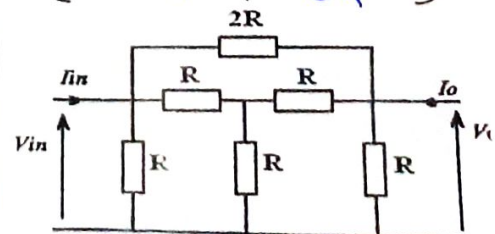$\frac{1}{V_{in}} = \frac{6R}{13}$ (2) $\frac{V_{in}}{I_{in}} = \frac{5}{13}$
 $\frac{I_{in}}{V_{in}} = -\frac{5}{13}$ $\frac{I_{in}}{V_{in}} = \frac{24}{13R}$




5 pts. **Exercise 3:** Lets consider the opposite circuit with **ideal** diode:

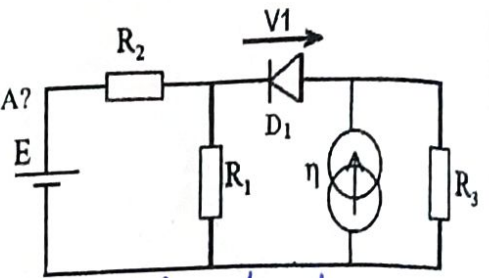- 1/ Remove the diode, then **determine** the dropping voltage V_1 ?
- 2/ **Determine** the current flowing R_3 , for $R_1=R_2=R_3=500\Omega$, $E=10v$, $\eta=20mA$?
- 3/ **Determine** the current flowing R_3 , if we reverse the diode?



1/

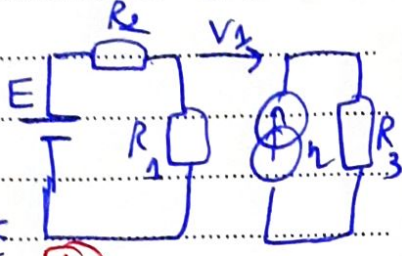
$$V_1 = R_3 \eta - \frac{R_1}{R_1 + R_2} E$$



2/ for $R_1=R_2=R_3=R$ we have

$$V_1 = R \eta - \frac{E}{2} = +5v > 0$$

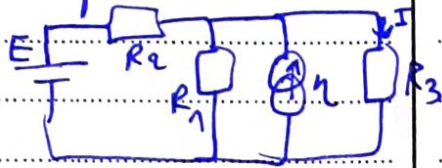\Rightarrow the diode is forward \Rightarrow short circuit



MILMAN

$$I = \frac{V_E}{R_3} = \frac{E + \eta R_3}{R_3 \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_3} \right)}$$

$$\Rightarrow I = \frac{R_1(E + R_3 \eta)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

$$I = \frac{20}{3} \text{ mA} = 6,6 \underline{6} \text{ mA}$$

3/ if we reverse the diode \Rightarrow

$$V_1 = -5v < 0 \Rightarrow D \text{ is reverse}$$

\Rightarrow open circuit

\Rightarrow the current flowing R_3 is $\eta = 20 \text{ mA}$

الاسم: _____
 الملقب: _____
 الشعبة: _____
 الفوج: _____



5 pts. **Exercise 4:** Lets consider the opposite amplifier circuit:

1/ **Determine** the base resistor R_b to have the operating point Q at the midpoint (middle) of the static charge.

Considering the equivalent AC circuit below:


2/ **Find** the voltage gain G_v , and the input impedance Z_{in} ?

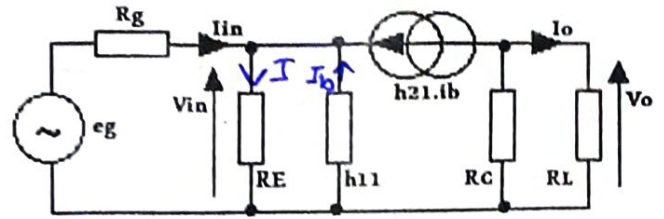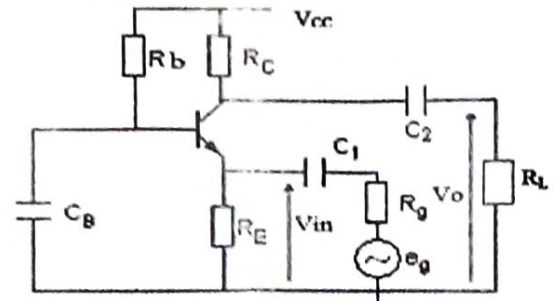Given: $R_g = 100\Omega$, $R_E = 1k\Omega$, $R_C = R_L = 10k\Omega$, $h_{11} = 5k\Omega$,
 $h_{21} = \beta = 100$, $h_{22} = 0$, $V_{be} = 0,6v$, $V_{cc} = 10v$.



The charge loop
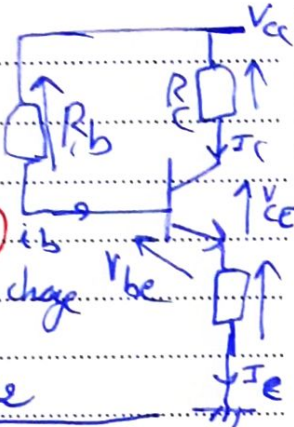
$$V_{CE} = V_{cc} - (R_C + \frac{\beta+1}{\beta} R_E) I_C$$



Q in the middle of static charge V_{be}

$$V_{CEQ} = \frac{V_{cc}}{2} \Rightarrow I_{CQ} = \frac{V_{cc}/2}{R_C + \frac{\beta+1}{\beta} R_E}$$

calculating $I_{CQ} = 0,454 \text{ mA}$
 then $I_{BQ} = \frac{I_{CQ}}{\beta} = 4,54 \mu\text{A}$

The attack loop

$$\Rightarrow I_B = \frac{V_{cc} - V_{be}}{R_b + (\beta+1) R_E}$$

the we have

$$R_b = \frac{V_{cc} - V_{be} - (\beta+1) R_E I_{BQ}}{I_{BQ}}$$

calculating $R_b = 1,97 \text{ M}\Omega$

We have $G_v = \frac{V_o}{V_{in}}$

$$V_{in} = -h_{11} I_B \quad \text{a) o.f.}$$

$$V_o = -\beta (R_C || R_L) I_B = -\frac{\beta R_C R_L}{R_C + R_L} I_B \quad \text{b) o.f.}$$

$$\frac{b}{a} \Rightarrow G_v = \frac{\beta R_C || R_L}{h_{11}} = \frac{\beta R_C R_L}{h_{11} (R_C + R_L)} \quad \text{o.f.}$$

calculating $G_v = 100 \quad \text{o.f.}$

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

$$\frac{1}{Z_{in}} = \frac{1}{R_E} + \left(\frac{\beta+1}{h_{11}} \right) \Rightarrow Z_{in} = R_E || \frac{h_{11}}{\beta+1} \quad \text{o.f.}$$

calculating $Z_{in} = 47,17 \Omega \quad \text{o.f.}$




الاسم: **B**
 اللقب:
 الشعبة:

Exam (1h:30min)
Fundamental Electronics 1

Sp. Exercise 1: Lets consider the opposite circuit :

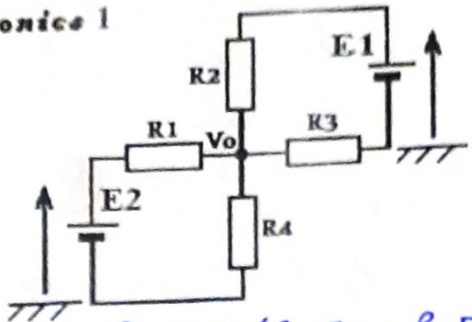Select one method to determinate the output voltage ?
 Choose from : (Superposition, Thevenin, or Milman)




MILMAN:

$$V_o = \frac{E_2 \times \frac{1}{R_2} + E_1 \times \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \quad (2)$$

$$V_o = \frac{R_3 R_4 (R_2 E_2 + R_1 E_1)}{R_2 R_3 R_4 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3} \quad (3)$$

Superposition

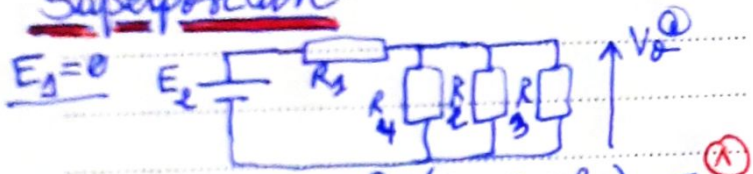

Voltage divider $\Rightarrow V_o^{(1)} = \frac{(R_2 \parallel R_3 \parallel R_4) E_2}{(R_2 \parallel R_3 \parallel R_4) + R_1}$

$$\Rightarrow V_o^{(1)} = \frac{R_2 R_3 R_4 E_2}{R_2 R_3 R_4 + R_1 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3} \quad (A)$$



Voltage divider $\Rightarrow V_o^{(2)} = \frac{(R_1 \parallel R_4 \parallel R_3) E_1}{(R_1 \parallel R_4 \parallel R_3) + R_2}$

$$\Rightarrow V_o^{(2)} = \frac{R_3 R_4 R_1 E_1}{R_2 R_3 R_4 + R_1 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3} \quad (B)$$

Sp. Exercise 2:


Lets consider the opposite quadrupole circuit :

1/ **Determinate** the admittance matrix **[Y]** using parallel association?

$$[Y] = [Y1] + [Y2] = \begin{pmatrix} \frac{1}{2R} + \frac{1}{R} = \frac{3}{2R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{3}{2R} \end{pmatrix} + \begin{pmatrix} \frac{2R}{3R^2} = \frac{2}{3R} & -\frac{R}{3R^2} = -\frac{1}{3R} \\ -\frac{1}{3R} & \frac{2}{3R} \end{pmatrix} = \begin{pmatrix} \frac{3}{2R} + \frac{2}{3R} = \frac{13}{6R} & -\frac{1}{R} - \frac{1}{3R} = -\frac{4}{3R} \\ -\frac{4}{3R} & \frac{13}{6R} \end{pmatrix} \quad (0,5)$$


2/ **Determinate** its hybrid matrix ? **[H]**
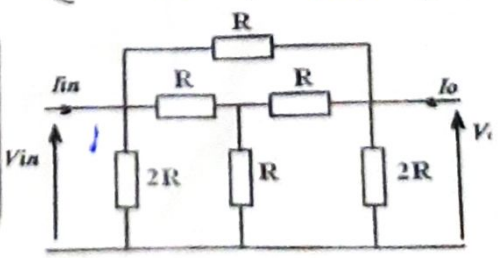
$$\begin{pmatrix} \frac{1}{Y_{11}} = \frac{6R}{13} & -\frac{V_{i2}}{Y_{11}} = \frac{8}{13} \\ \frac{V_{e1}}{Y_{11}} = -\frac{8}{13} & \frac{\Delta Y}{Y_{11}} = \frac{35}{26R} \end{pmatrix} \quad (2)$$




5 pts. **Exercise 3:** Lets consider the opposite circuit with ideal diode:

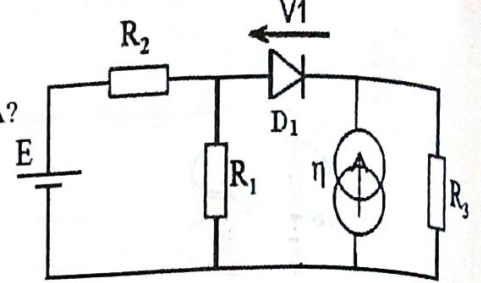- 1/ Remove the diode, then determinate the dropping voltage V_1 ?
- 2/ Determinate the current flowing R_3 , for $R_1=R_2=R_3=500\Omega$, $E=10v$, $\eta=20mA$?
- 3/ Determinate the current flowing R_3 , if we reverse the diode?



1/

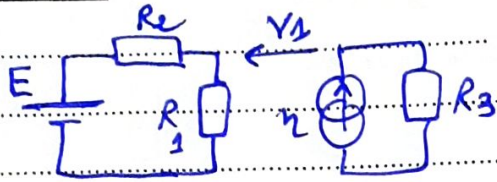

$$V_1 = \frac{R_1}{R_1 + R_2} E - R_3 \eta \quad (\text{A})$$

2/ for $R_1=R_2=R_3=R$ we have

$$V_1 = \frac{E}{2} - R\eta = -5v < 0 \quad (\text{A})$$


\Rightarrow the diode is reverse \Rightarrow Open circuit

\Rightarrow the current flowing R_3 is $\eta = 20mA$ (A)

3/ if we reverse the diode \Rightarrow

$$V_1 = R_3 \eta - \frac{R_1}{R_1 + R_2} E = +5v > 0 \quad (\text{A})$$

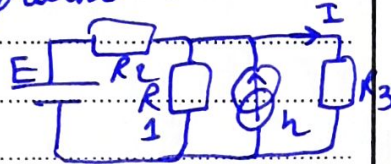\Rightarrow the diode is forward \Rightarrow short circuit



MILMAN

$$I = \frac{V_1}{R_3} = \frac{E + R_2 \eta}{R_3 \left(\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_3} \right)}$$

$$\Rightarrow I = \frac{R_1 (E + R_2 \eta)}{R_1 R_3 + R_2 R_3 + R_1 R_2} \quad (\text{A})$$

$$I = \frac{20}{3} mA = 6,66 mA$$

الاسم: _____
 اللقب: _____
 الفوج: _____
 الشعبة: _____



Exercice 4: Lets consider the opposite amplifier circuit:

1/ **Determine** the base resistor R_b to have the operating point Q at the midpoint (middle) of the static charge.


Considering the equivalent AC circuit below:

2/ **Find** the voltage gain G_v and the input impedance Z_{in} ?

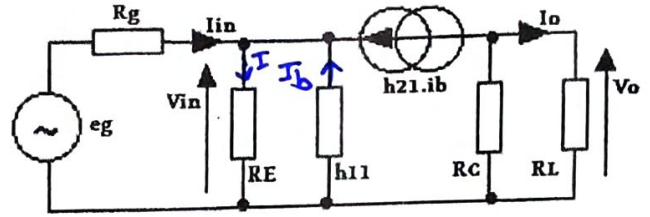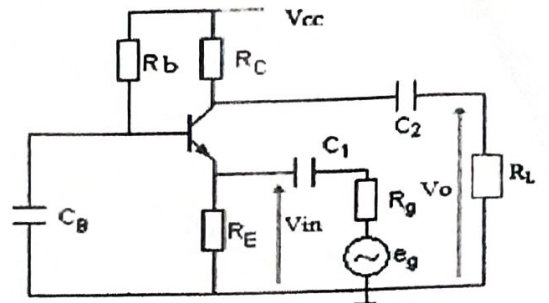Given: $R_g=100\Omega$, $R_E=1k\Omega$, $R_C=R_L=10k\Omega$, $h_{11}=5k\Omega$, $h_{21}=\beta=100$, $h_{22}=0$, $V_{be}=0,6v$, $V_{cc}=20v$.



the charge loop

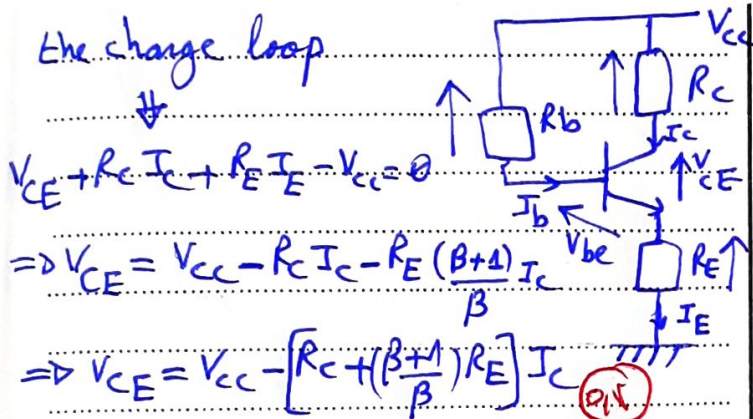

$$V_{CE} + R_C I_C + R_E I_E - V_{CC} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - R_C I_C - R_E (\beta + 1) I_B$$

$$\Rightarrow V_{CE} = V_{CC} - \left[R_C + (\beta + 1) R_E \right] I_C$$

Q in the middle of static charge.

$$\Rightarrow V_{CE0} = \frac{V_{CC}}{2} \Rightarrow I_{C0} = \frac{V_{CC} - V_{CE0}}{R_C + (\beta + 1) R_E}$$

calculating $\Rightarrow I_{C0} = 0,908 \text{ mA}$

then $I_{B0} = \frac{I_{C0}}{\beta} = 9,08 \mu\text{A}$

the attack loop $\Rightarrow V_{CC} - R_b I_b - V_{be} - R_E I_E = 0$

$$\Rightarrow V_{CC} - V_{be} = [R_b + (\beta + 1) R_E] I_b$$

then we have $R_b = \frac{V_{CC} - V_{be} - (\beta + 1) R_E I_b}{I_b}$

calculating: $R_b = 2,04 \text{ M}\Omega$

We have $G_v = \frac{V_o}{V_{in}}$

$V_{in} = -h_{11} \times I_b$

$V_o = -\beta I_b \times (R_C \parallel R_L) = -\beta \frac{R_C R_L}{R_C + R_L} \times I_b$

$\Rightarrow G_v = +\beta \frac{R_C R_L}{h_{11} (R_C + R_L)}$

Calculating $G_v = 100$

$Z_{in} = \frac{V_{in}}{I_{in}}$

We have KCL $\Rightarrow I_{in} + \beta I_b + I_b = I$

$\Rightarrow I_{in} = I - (\beta + 1) I_b$

$I = \frac{V_{in}}{R_E} \Rightarrow I_{in} = \frac{V_{in}}{R_E} - (\beta + 1) I_b$

$\Rightarrow I_b = \frac{V_{in}}{h_{11}}$

$I_{in} = \frac{V_{in}}{R_E} + \frac{V_{in} (\beta + 1)}{h_{11}} \Rightarrow \frac{I_{in}}{V_{in}} = \frac{1}{R_E} + \frac{(\beta + 1)}{h_{11}}$

$\Rightarrow \frac{1}{Z_{in}} = \frac{1}{R_E} + \frac{(\beta + 1)}{h_{11}} \Rightarrow Z_{in} = R_E \parallel \frac{h_{11}}{\beta + 1}$

calculating: $Z_{in} = 47,17 \Omega$