



Module: Fundamental Electrical Engineering 1

L2 ST

Dr: M. Bouzidi / Dr: M. Korichi

Exam (1h :30 min)

اللقب:
الاسم:
الشعبة:
الفوج:

* 
20

Exercise 1 (6 pts)


Using the mesh analysis, find J_1 , J_2 and J_3 .

Deduce the voltage V_y .

$$I = 12 \text{ A}, R = 10 \Omega.$$

Solution.

Mesh (1):  0.75 pt

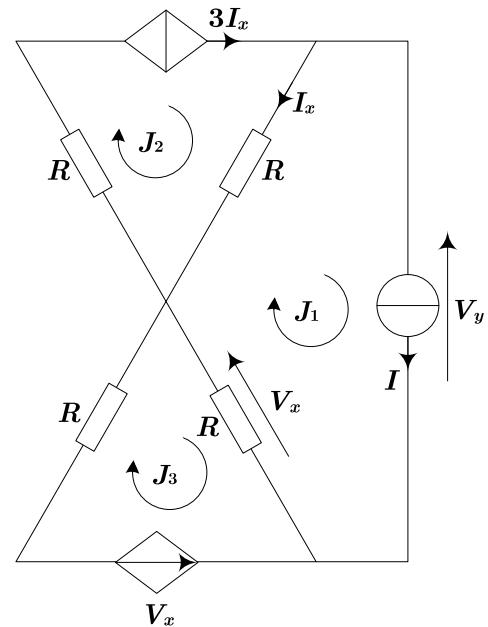

Mesh (2):

0.75 pt

Mesh (3):

0.75 pt

$$I_x = \dots \quad V_x = \dots \quad V_y = \dots$$

0.5 pt

0.5 *pt*

0.75 nt.

0.5 pt

0.5 nt

0.5 nt

$$J_1 = \dots = A$$

$J_2 = \dots \dots \dots A$


$$J_3 \equiv_{\text{weakly}} A$$

$$V_e = \dots \dots V$$

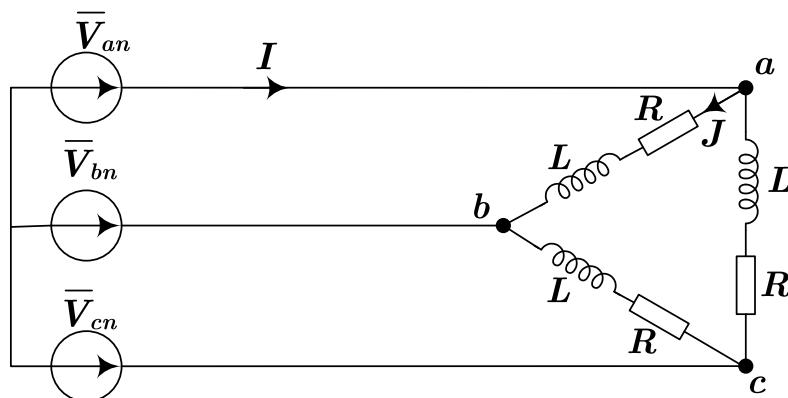Exercise 3 (6 pts)

The three-phase balanced system 220/380V 50Hz in the figure below supplies a three inductive impedances $\bar{Z} = 50\angle 45^\circ \Omega$ contains $R=?$, $L=100\text{ mH}$.

- 1- What is the type of connection?
- 2- What the voltage across each impedance.
- 3- Calculate the value of the resistance R .
- 4- Calculate the phase current \mathbf{J} , the line current \mathbf{I} , and the power factor.
- 5- Calculate the active power P , reactive Q , and apparent power S .
- 6- Calculate the capacitor coupled in delta that raises the power factor to 1.
- 7- In the phasor diagram showing below, represent the vectors : \mathbf{U}_{ab} , \mathbf{U}_{bc} , \mathbf{U}_{ca} , \mathbf{J}_{ab} , \mathbf{J}_{bc} , \mathbf{J}_{ca} .



Solution

1- The type of connection is : 0.25 pt

2- The voltage across each impedance is V 0.25 pt

3- Calculation of resistance R :

$$R = \dots, [R = \dots \Omega],$$

0.25 pt

0.25 pt

4- Calculation of the phase current \mathbf{J} , line current \mathbf{I} , and the power factor PF .

$$J = \dots, [J = \dots A],$$

0.25 pt

$$I = \dots, [I = \dots A], PF = \dots, [PF = \dots]$$

0.25 pt

0.25 pt

0.25 pt

0.25 pt

5- Powers calculation

- $P = \dots$, $P = \dots W$

0.25 pt

- $Q = \dots$, $Q = \dots$ Var

0.25 pt

- $$S = \dots, S = \dots VA$$

0.25 pt

6- Capacitor calculation

- $C = \dots$, $\mathcal{C} = \dots F$

0.25 pt

7- Phasor diagram, Representation of the vectors: U_{ab} , U_{bc} , U_{ca} , J_{ab} , J_{bc} , J_{ca}

