

Power Electronics

Dr : M. Bouzidi

L3 Automation


**Exam**

01/02/2024 Duration : 1h :30 min

<p><b>Full name:</b> .....</p> <p><b>Groupe:</b> .....</p>	<p><b>Note:</b> <u>    20    </u></p> <p>*</p>
--	--

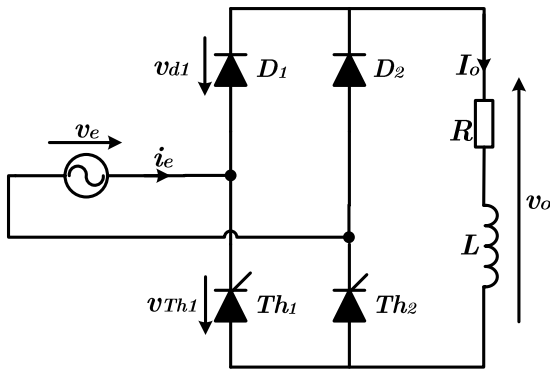**Exercise 1: (7 pts)** The controlled Full-wave rectifier supplies an inductive load  $R-L$ . The load current is constant due to the large value of the inductance  $I_o=10A$ .

The input voltage RMS is  $V_{e,rms} = 220V$ . For  $\alpha = \frac{\pi}{3}$  :



- 1- Determine the conduction intervals of the power switches.
- 2- Represent the waveforms of  $v_o$ ,  $i_e$ ,  $v_{Th1}$ , and  $v_{d1}$ .
- 3- Calculate the average value of the output voltage.
- 4- Calculate the RMS value of the input current.
- 5- Calculate the active power, apparent power and the power factor.

**Solution**

1- Conduction intervals

- $Th_1$  ON:  $\theta \in$  .....
- $Th_2$  ON:  $\theta \in$  .....
- $D_1$  ON:  $\theta \in$  .....
- $D_2$  ON:  $\theta \in$  .....

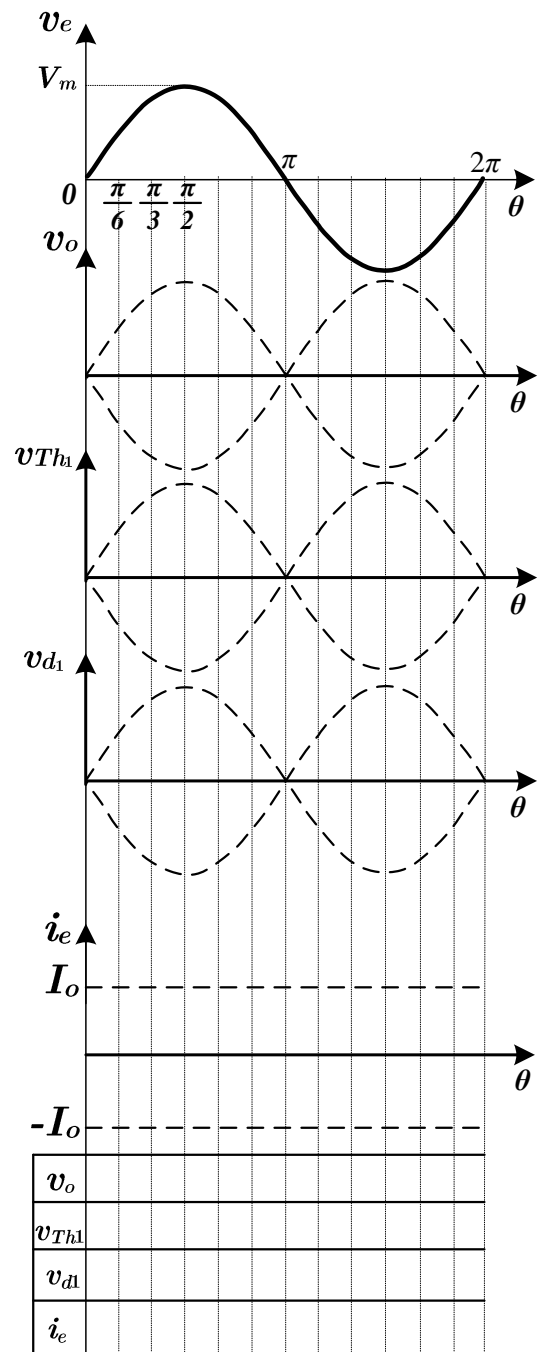


Figure (1)

2- Waveforms representation:

Complete the table under **Figure (1)** for the variables  $v_o$ ,  $i_e$ ,  $v_{Th1}$ ,  $v_{d1}$ .

3- Average value of the output voltage:

$\bar{V}_o = \dots\dots\dots$	$\bar{V}_o = \dots\dots\dots$ ,	$\bar{V}_o = \dots\dots\dots V$
-------------------------------	---------------------------------	---------------------------------

4- RMS value of the input current:

$I_{e,rms}^2 = \dots\dots\dots$	$I_{e,rms} = \dots\dots\dots$ ,	$I_{e,rms} = \dots\dots\dots A$
---------------------------------	---------------------------------	---------------------------------

5- Active power, apparent power, power factor:

• $P = \dots\dots\dots$	$P = \dots\dots\dots$ ,	$P = \dots\dots\dots W$
-------------------------	-------------------------	-------------------------

• $S = \dots\dots\dots$	$S = \dots\dots\dots$ ,	$S = \dots\dots\dots VA$
-------------------------	-------------------------	--------------------------


• $PF = \dots\dots\dots$ ,	$PF = \dots\dots\dots$
----------------------------	------------------------

**Exercise 2: (6pts)**

The controlled three-phase half-wave rectifier supplies an inductive load  $R-L$ . The load current is constant due to the large value of the inductance.

The input voltage RMS is

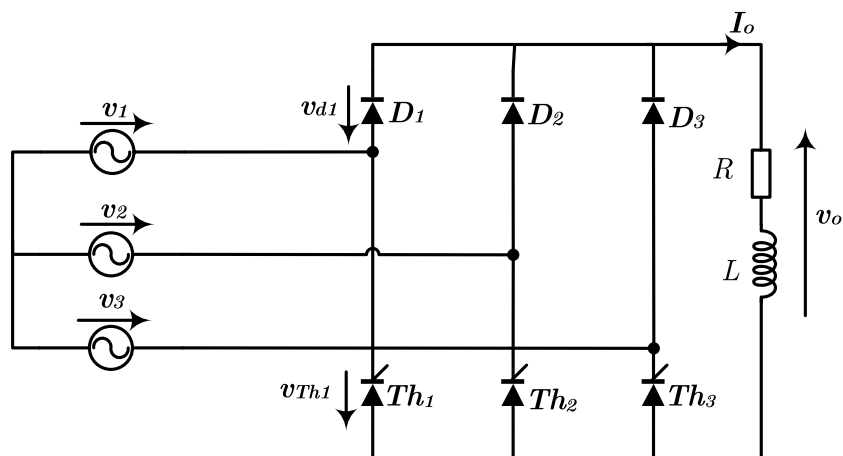$V_{e,rms} = 220V$ . For  $\alpha = \frac{\pi}{6}$ .



1- Determine the conduction intervals of the power switches.

2- Represent the waveforms of  $v_o$ ,  $v_{Th1}$  and,  $v_{d1}$ .


**Solution**

1- Conduction intervals

- $Th_1$  ON:  $\theta \in \dots\dots\dots$                        $D_1$  ON:  $\theta \in \dots\dots\dots$
- $Th_2$  ON:  $\theta \in \dots\dots\dots$                        $D_2$  ON:  $\theta \in \dots\dots\dots$
- $Th_3$  ON:  $\theta \in \dots\dots\dots$                        $D_3$  ON:  $\theta \in \dots\dots\dots$

2- Waveforms representation

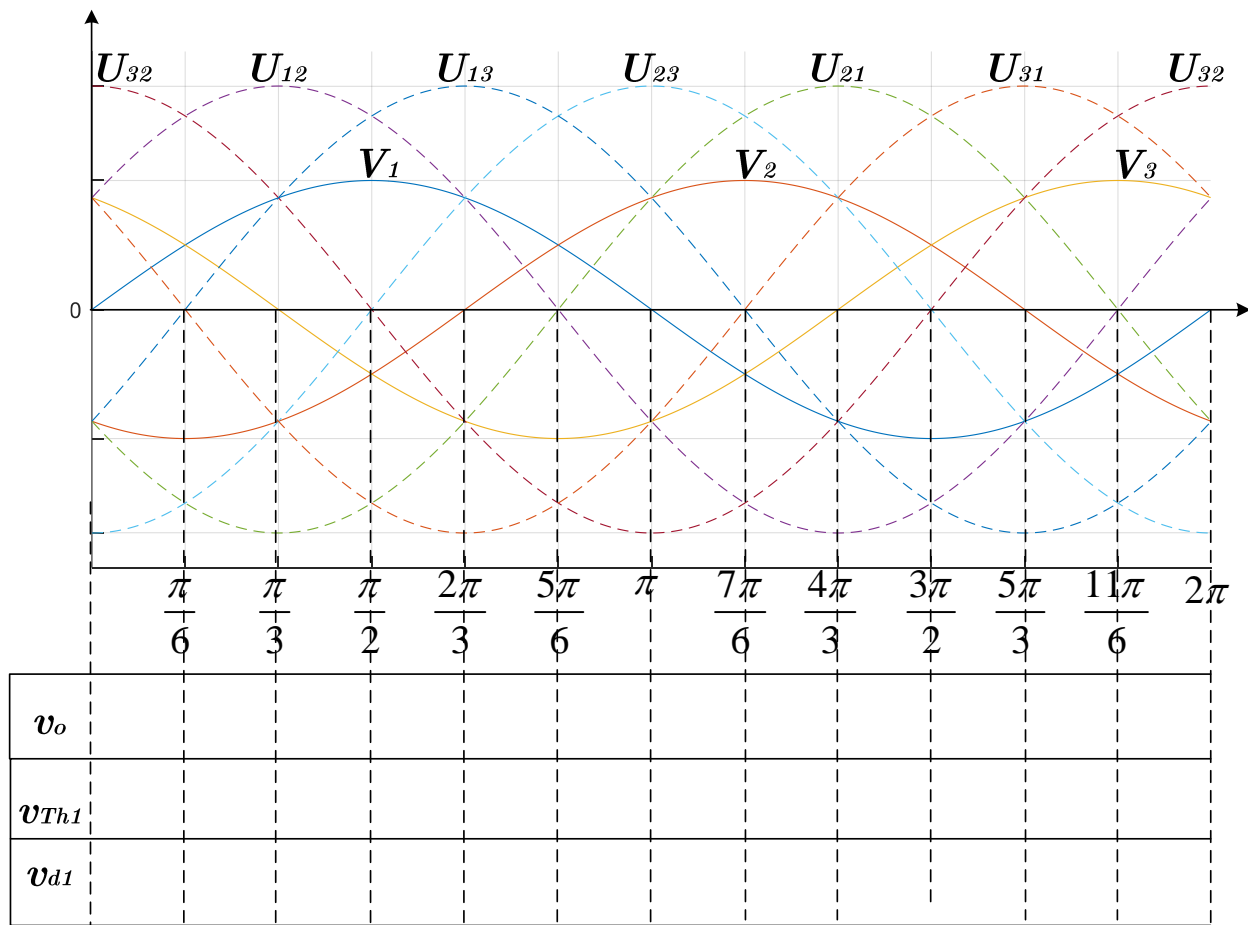Complete the table below for the variables  $v_o$ ,  $v_{Th1}$ ,  $v_{d1}$ .



**Exercise 3 (7 pts)**

The DC-DC converter shown below is operated in a continuous conduction mode. The transistor is turned ON over the interval  $[0 \ D T_s]$ , where  $T_s$  is the switching period, and  $D$  is its duty cycle. The capacitance  $C$  is assumed to have a sufficient value to keep the output voltage constant.


- 1- What is the type of this converter (Buck or Boost).
- 2- Represent the following waveforms over one period:  $i_L(t)$ ,  $v_L(t)$ ,  $v_d(t)$  and  $v_H(t)$ .
- 3- Calculate the average value of  $v_d$  as a function of  $E$  and  $D$ .

4- Express the output voltage  $V_o$  in terms of  $D$  and  $E$ .

5- Calculate the average value of the input current in terms of  $E$ ,  $R$ , and  $D$ .

**Solution**

1- The type of this converter is: .....

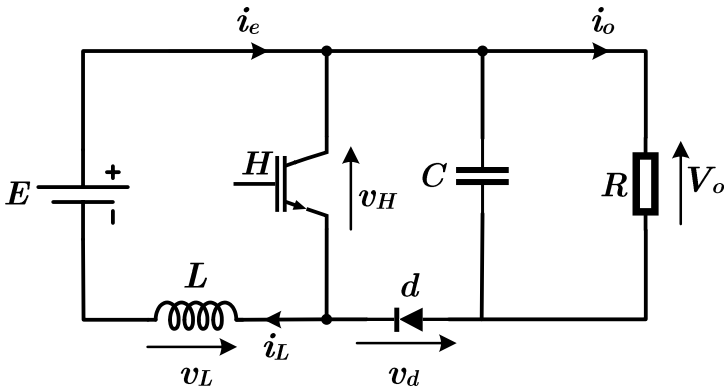

2- Waveforms representation:

Complete the table below for variables:

$v_H$ ,  $v_d$ ,  $v_L$ , and  $i_L$  and represent them.

3- Average value of  $v_d$

$\bar{V}_d = \dots\dots\dots$

$\bar{V}_d = \dots\dots\dots$

4-  $V_o = f(E, D) = ?$

.....  
 .....

$V_o = \dots\dots\dots$

5-  $\bar{I}_e = f(E, D) = ?$

.....  
 .....

$\bar{I}_e = \dots\dots\dots$

