

2- Waveforms representation:

Complete the table under **Figure (1)** for the variables v_o , i_e , v_{Th1} , v_{d1} .

3- Average value of the output voltage:

$$\bar{V}_o = \frac{1}{\pi} \int_{\pi/3}^{\pi} V_m \sin \theta \, d\theta \quad 0,25 \quad \bar{V}_o = \frac{3 V_m}{2\pi} \quad 0,25 \quad \bar{V}_o = 148,62 \text{ V} \quad 925$$

4- RMS value of the input current:

$$I_{e,rms}^2 = \frac{1}{2\pi} \left[\int_{\pi/3}^{\pi} I_o^2 \, d\theta + \int_{4\pi/3}^{2\pi} (I_o)^2 \, d\theta \right] \quad 0,25 \quad I_{e,rms} = \sqrt{\frac{2}{3}} I_o \quad 0,25 \quad I_{e,rms} = 8,16 \text{ A}$$

5- Active power, apparent power, power factor:

$$P = \bar{V}_o \cdot I_o \quad 0,25 \quad P = \frac{3}{2\pi} V_m \cdot I_o \quad 0,25 \quad P = 1486,2 \text{ W}$$

$$S = V_{e,rms} \cdot I_{e,rms} \quad 0,25 \quad S = V_{e,rms} \cdot \sqrt{\frac{2}{3}} I_o \quad 0,25 \quad S = 1795,2 \text{ VA}$$


$$PF = \frac{P}{S} \quad 0,25 \quad PF = 0,82 \quad 0,25$$

Exercise 2: (6pts)

The controlled three-phase half-wave rectifier supplies an inductive load $R-L$. The load current is constant due to the large value of the inductance.

The input voltage RMS is
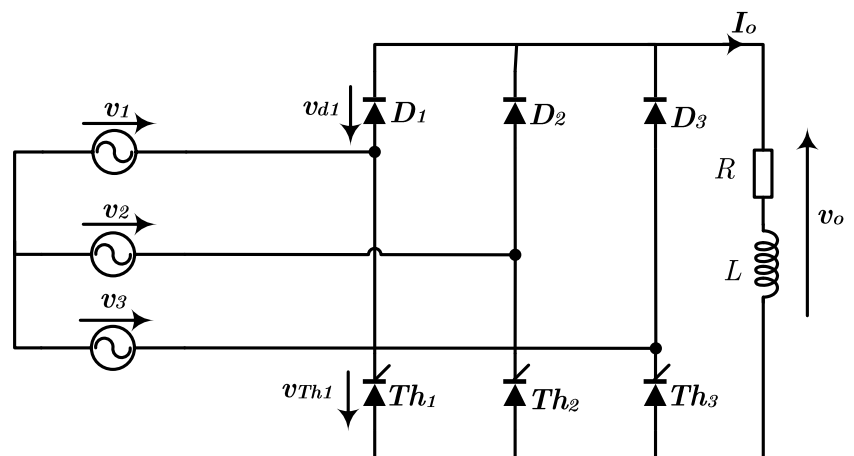
$$V_{e,rms} = 220V. \text{ For } \alpha = \frac{\pi}{6}.$$



1- Determine the conduction intervals of the power switches.

2- Represent the waveforms of v_o , v_{Th1} and, v_{d1} .


Solution

1- Conduction intervals

- Th_1 ON: $\theta \in [4\pi/3, 2\pi]$ (0,5)
- Th_2 ON: $\theta \in [0, 2\pi/3]$ (0,1)
- Th_3 ON: $\theta \in [2\pi/3, 4\pi/3]$ (0,5)
- D_1 ON: $\theta \in [\pi/6, 5\pi/6]$ (0,5)
- D_2 ON: $\theta \in [5\pi/6, 3\pi/2]$ (0,1)
- D_3 ON: $\theta \in [3\pi/2, 2\pi] \cup [0, \pi/6]$ (0,5)

2- Waveforms representation

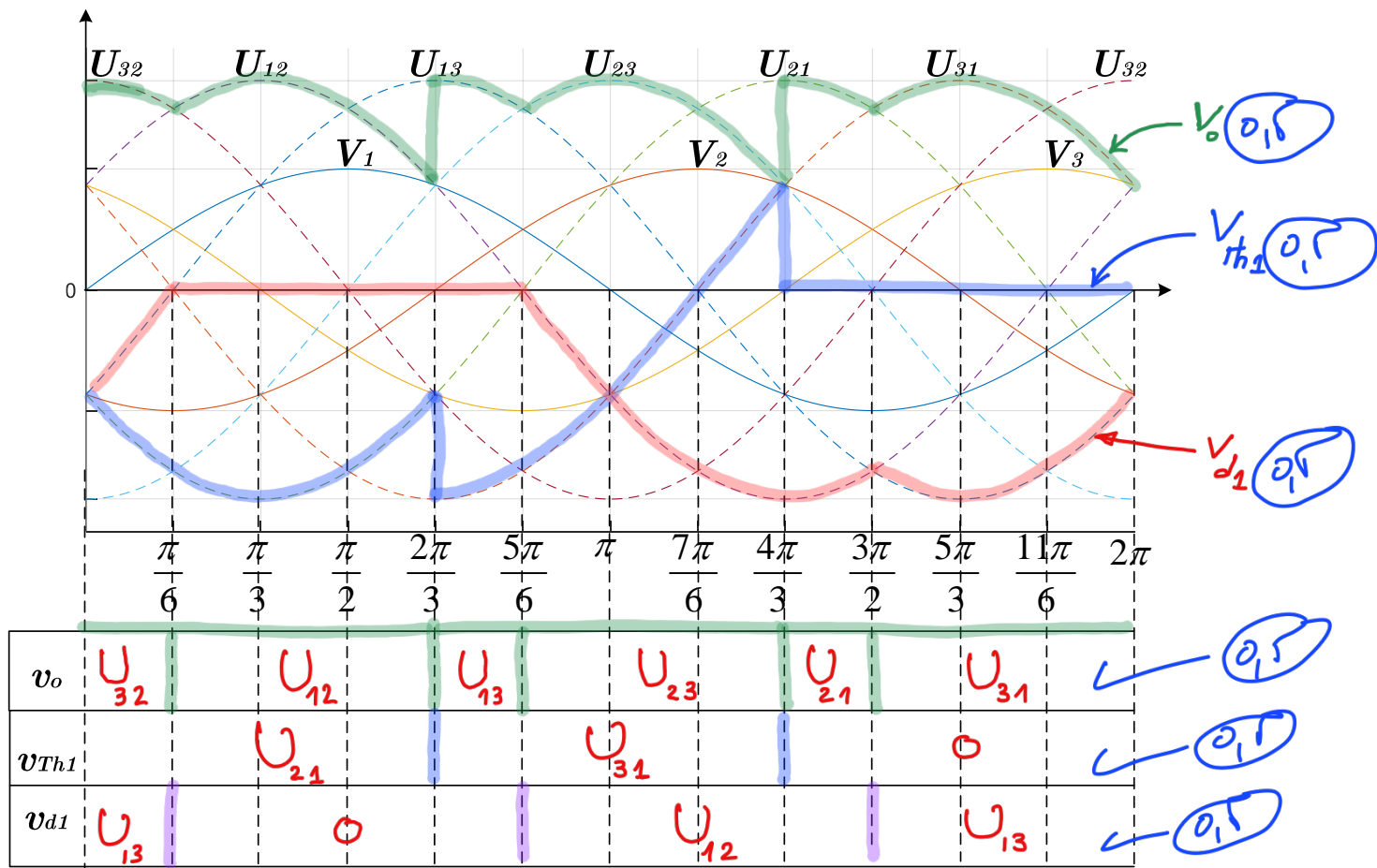Complete the table below for the variables v_o , v_{Th1} , v_{d1} .



Exercise 3 (7 pts)

The DC-DC converter shown below is operated in a continuous conduction mode. The transistor is turned ON over the interval $[0, DT_s]$, where T_s is the switching period, and D is its duty cycle. The capacitance C is assumed to have a sufficient value to keep the output voltage constant.


- 1- What is the type of this converter (Buck or Boost).
- 2- Represent the following waveforms over one period: $i_L(t)$, $v_L(t)$, $v_d(t)$ and $v_H(t)$.
- 3- Calculate the average value of v_d as a function of E and D .

4- Express the output voltage V_o in terms of D and E .

5- Calculate the average value of the input current in terms of E , R , and D .

Solution

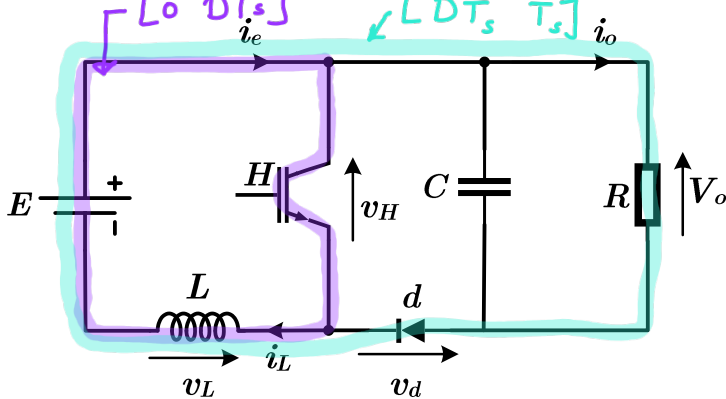1- The type of this converter is: *Boost* (0.5)



2- Waveforms representation:

Complete the table below for variables:

v_H , v_d , v_L , and i_L and represent them.

3- Average value of v_d

$$\bar{V}_d = \frac{1}{T_s} \int_0^{DT_s} -V_o dt$$

$$\bar{V}_d = -D \cdot V_o \quad \text{(0.5)}$$

4- $V_o = f(E, D) = ?$ By applying KVL:

$$E - V_o - V_d - V_L = 0$$


$$\Rightarrow \bar{V}_o = V_o = E - \bar{V}_d \quad \text{(0.5)}$$

$$V_o = \frac{E}{1-D} \quad \text{(0.5)}$$

5- $\bar{I}_e = f(E, D) = ?$

$$\bar{I}_o = \frac{V_o}{R} = (1-D) \cdot \bar{I}_e$$
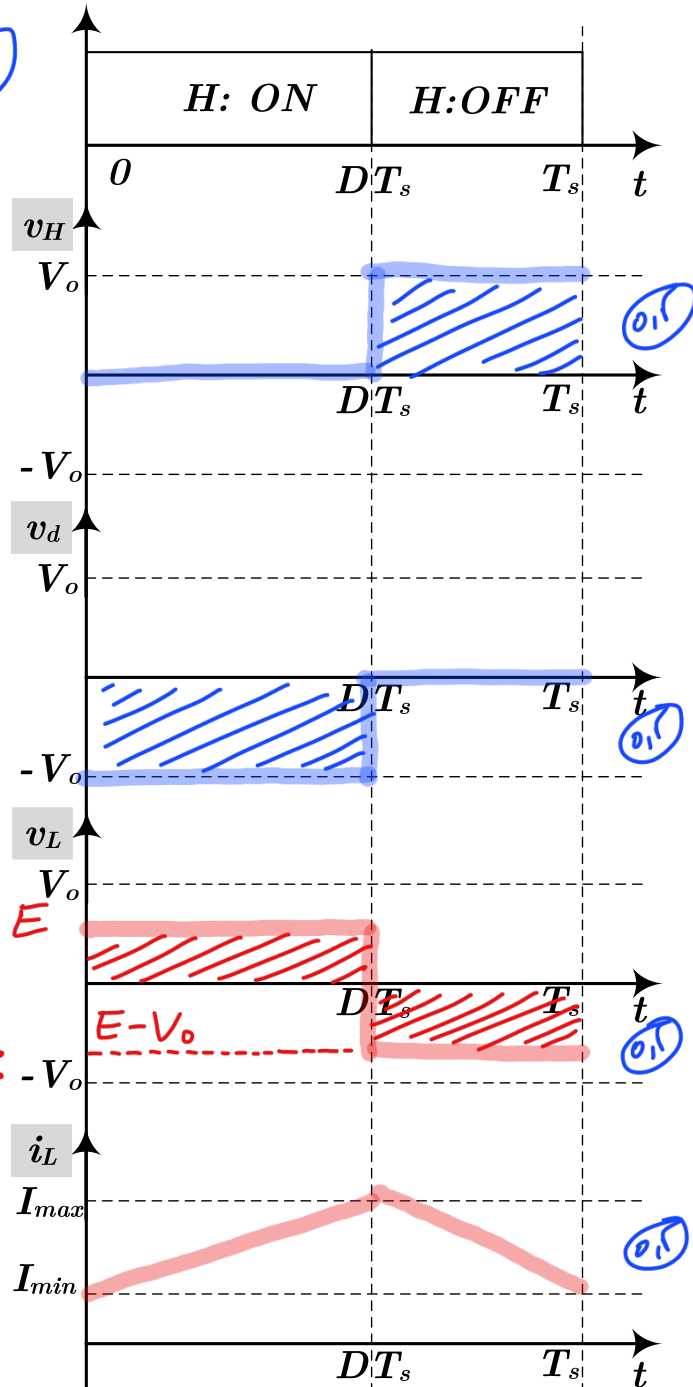
$$\bar{I}_e = \frac{E}{R(1-D)^2} \quad \text{(0.5)}$$



v_H	0	V_o	(0.5)
v_d	$-V_o$	0	(0.5)
v_L	E	$E - V_o$	(0.5)
i_L	$\frac{E}{L} \cdot t + I_{min}$	$\frac{E - V_o}{L} (t - DT_s) + I_{max}$	(0.5)

